

ATIVIDADE - MAPAS DE KARNAUGH

1) Simplifique essas funções, usando mapa de Karnaugh:

a) $S = \bar{A} \cdot B \cdot C + \bar{A} \cdot \bar{C} + A \cdot C$

b) $S = \bar{A} \cdot B \cdot C \cdot \bar{D} + \bar{A} \cdot B \cdot \bar{C} \cdot D + \bar{A} \cdot B \cdot \bar{C} \cdot \bar{D} + \bar{A} \cdot \bar{B} \cdot C \cdot D + \bar{A} \cdot \bar{B} \cdot C \cdot \bar{D}$

2) Elabore a equação booleana simplificada das seguintes tabelas-verdade, usando mapa de Karnaugh:

a)

A	B	C	S
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

b)

A	B	C	S
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

c)

A	B	C	S
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

3) Simplifique:

a) $f(A, B, C) = \sum_m(0, 3, 4, 6)$

b) $f(A, B, C, D) = \sum_m(1, 3, 7)$

c) $f(A, B, C, D) = \sum_m(10, 8, 7, 14)$

d) $f(A, B, C, D) = \sum_m(2, 4, 6, 8, 10, 12, 14)$